

KEY

[25 Points, a-g 3 points each, h 4 points] 1. Simplify each of the following expressions to minimum SOP form.

- $f(a,b,c,d) = (b'+c'+d)(a'+b'+c')(a+b+c)(b+c+d)$
- $f(a,b,c) = xy + x'yz' + yz$
- $f(w,x,y,z) = w'x'y'+w'xz'+[(x+y+w'z)(x'+z'+wy)']$
- $f(w,x,y,z) = wxy'+(w'y' \equiv x) + (y \oplus wz)$. Recall $a \oplus b = a'b + ab'$, and $(a \equiv b) = (a \oplus b)'$
- $f(u,v,w,x,y,z) = (v'+u+w)(wx+y+uz') + (wx+uz'+y)$
- $f(w,x,y,z) = (w+x')(y+z')(w+y)(x+y)(w+z)(x+z)$
- Use QM to simplify 1b. Show your work for full credit.
- $f(a,b,c,d) = a'bc'd + a'b'd + a'cd + abd + abc$.
Assume that ABCD = 0101, ABCD = 1001, ABCD = 1011 never occur.

(g) $xy + x'yz' + yz =$

xy	$x'yz'$	yz	$=$
$x y z + x y z'$	$+ x' y z' + x y z + x' y z'$		
\downarrow	\downarrow	\downarrow	
111	110	010	
(7)	(6)	(3)	
Column I	Column II	Column III	
(2) 010	(2,5) 01-	(2,5,6,7) -1-	$\rightarrow y$
(3) 011	(2,6) -10	(2,6,3,7) -1-	
(6) 110	(3,-) -11		
(7) 111	(6,-) 11-		

$xy z$
 $x y z'$
 $x' y z'$
 $x y z$
 $x' y z$


(h)

ab	00	01	11	10
01				
00				
01	1	X	1	X
11	1	1	1	X
10				


$\rightarrow \underline{d + abc}$

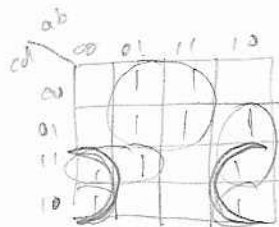(a) $f = (b'+c'+d)(b'+c'+a')(b+c+a)(b+c+d)$
 use $(x+y)(x+z) = x+yz$


$$= (b'+c'+a'd)(b+c+ad) = b'b + b'c + b'ad + c'b + c'c + c'ad + a'db + a'dc + a'dad$$


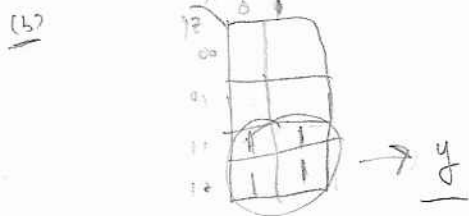
$$= \underline{b'c + a'cd + ab'd + bc'}$$




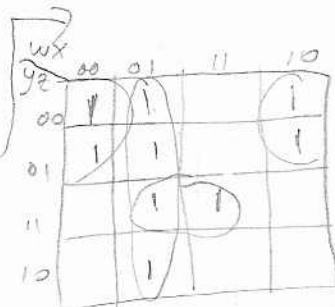(c) $[(x+y+wz)(x'+z'+wy')]'$
 $(x+y+wz)' + (x'+z'+wy')' =$
 $x'y'(wz)' + xz'(wy)'$
 $x'y'(wz) + xz'(w+y) =$
 $x'y'w + x'y'z' +$
 $xzw' + xzy$



(d) note $a \oplus b = (a'b + ab')' = (a+b')(a'+b) = ab + a'b'$
 $t = wxy' + (w'y'x + (w'y')'x') + y'wz + y(wz)'$
 $= wxy' + w'y'x + (w+y)x' + y'wz + y(w'+z')$

$$= w'x + x'yz + x'y'$$

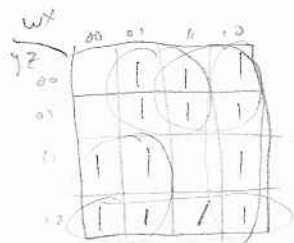

$$\Rightarrow \underline{yz' + wx' + w'y + x'y'}$$

(e) $f = (wx + yz)(v' + u + w + 1) = \underline{wx + yz}$

(f) $(w+x')(y+z')(w+y)(x+z)(w+z)(x+z)$

$$(w+y)(w+z) = w+yz$$

$$(x+w)(x+z) = x+yz$$


$$= (w+x')(y+z')(w+yz)(x+yz)$$

$$= (w+x'yz)(y+z')(x+yz)$$

$$= (wy + wz' + x'yz + x'yz'z')(x+yz)$$

$$= (wy + wz' + x'yz)(x+yz)$$
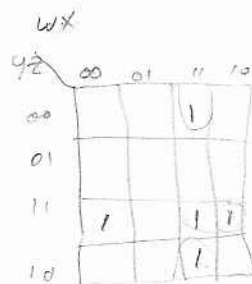
$$= (wyx + wyyz + wz'x + wz'yz + x'yzx + x'yzyz)$$



$$= wyx + wyz + wxz' + x'yz$$

[26 Points] 2. A combinational network has four inputs (A, B, C, and D), which represent a binary coded decimal digit. The network has two groups of outputs – S, T, U, V, and W, X, Y, Z. Each group represents a BCD digit. The output digits represent a decimal number which is 5 times the input number. For example, if ABCD = 0111, the outputs are 0011 0101. Assume that invalid BCD digits do not occur as inputs (this assumption ought to be reflected in the truth table).

[10] (a) Construct the truth table.

this is problem 5.27 from the homework

	A	B	C	D	S	T	U	V	W	X	Y	Z
0)	0	0	0	0	0	0	0	0	0	0	0	0
1)	0	0	0	1	0	0	0	0	0	1	0	1
2)	0	0	1	0	0	0	0	1	0	0	0	0
3)	0	0	1	1	0	0	0	1	0	1	0	1
4)	0	1	0	0	0	0	1	0	0	0	0	0
5)	0	1	0	1	0	0	1	0	0	1	0	1
6)	0	1	1	0	0	0	1	1	0	0	0	0
7)	0	1	1	1	0	0	1	1	0	1	0	1
8)	1	0	0	0	0	1	0	0	0	0	0	0
9)	1	0	0	1	0	1	0	0	0	1	0	1
	1	0	1	0	X	X	X	X	X	X	X	X
	1	0	1	1								
	1	1	0	0								
	1	1	0	1								
	1	1	1	0								
	1	1	1	1								


don't care - invalid digits never occur

(b) From inspection:

$$\begin{aligned}
 S &= 0 & W &= 0 \\
 T &= A & X &= D \\
 U &= B & Y &= 0 \\
 V &= C & Z &= D
 \end{aligned}$$

(can do Kmap instead)

(c)

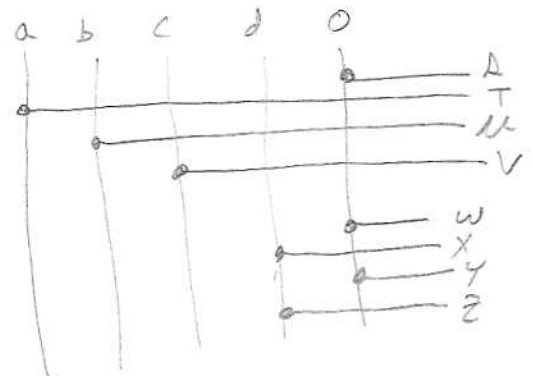


[24 Points] 3. Complete the following conversion problems.

- a. Write $wxy'+w'x'z+wy'z+w'yz'$ in minimal POS form.
- b. Given $f'(a,b,c,d) = \prod M(0,1,2,3,7,9,15)$, find the minterm expansion for f (algebraic form)
- c. Given $f(a,b,c,d) = \sum m(0,1,4,5,10,12) + \sum d(1,2,3,4)$, write f in minimum POS form.
- d. Given $f(a,b,c,d) = \prod M(0,1,2,3,7,9,15)$, write f in minimum SOP form.
- e. Draw $wxy'+w'x'z+wy'z'$ using only NAND gates.
- f. Draw $wxy'+w'x'z+wy'z'$ using only NOR gates.
- g. Convert $f(a,b,c,d) = \sum m(0,1,4,5,10,12) + \sum d(1,2,3,4)$ to minimum SOP form.
- h. Convert 1f into POS form.

(b)

3/a)

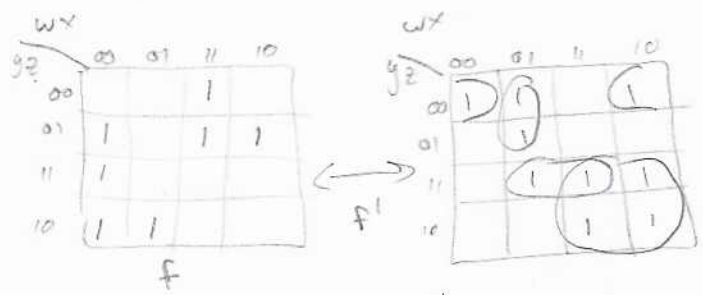


$$f' = wy + xy + z + w'x'y' + x'y'z'$$

$$f = (f')' = (w'y')(x'+y'+z')(w+x+y)(x+y+z)$$

(b) $f' = \sum m(4, 5, 6, 8, 10, 11, 12, 13, 14)$ and $f = \sum m(0, 1, 2, 3, 7, 9, 15)$
 $= a'b'c'd' + a'b'c'd + a'b'cd' + a'b'cd + a'bcd + a'b'cd' + abcd$

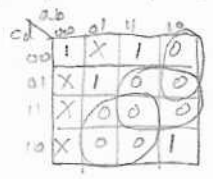
(c) $f = \sum m(0, 5, 10, 12) + \sum d(1, 2, 3, 4)$





$$f' = bc + ad + ab'c'$$

$$f = (b'+c')(a'+d')(a'+b+c)$$

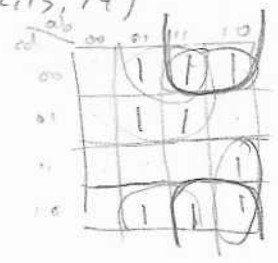(d) $f = \sum m(4, 5, 6, 8, 10, 11, 12, 13, 14)$



$$\rightarrow bc' + bd' + a'd' + ab'e$$

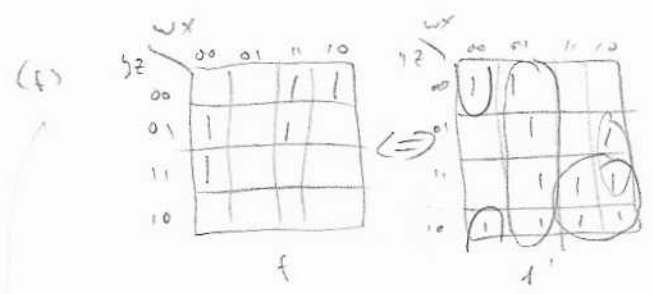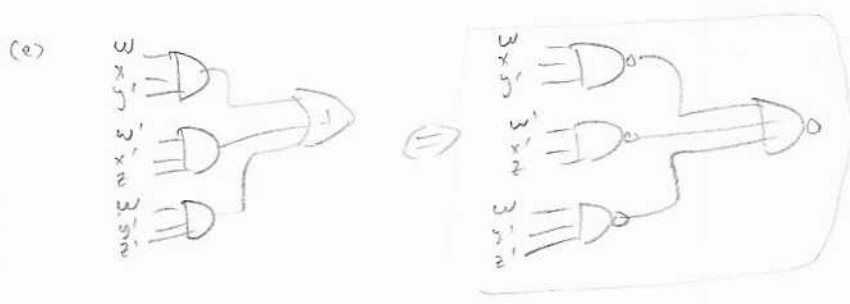


$$f' = w'x + wy + wx'z + w'x'z'$$

$$f = (w+x')(w+y)(w'+x+z')(w+x+z)$$

(g) this is the same function as (c)



$$f = b'cd' + a'c' + bc'd'$$

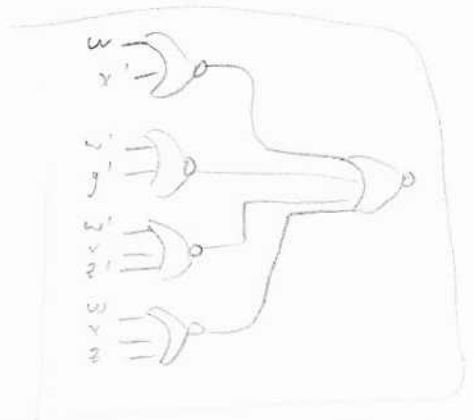

(h) already in POS form!

[25 Points] 4. A combinational network has four input bits A, B, C, and D. You are to design a network with an output Z (which consists of multiple bits). Z is a binary number whose value represents the number of 1's in the input. For example, if ABCD = 1001, the bits of Z represent the number 2.


[2] (a) How many bits must Z have?

3 bits

[10] (b) Construct a truth table for the bits of Z.


a	b	c	d	z_1	z_2	z_3
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	0
0	1	1	1	0	1	1
1	0	0	0	0	0	1
1	0	0	1	0	1	0
1	0	1	0	0	1	0
1	0	1	1	0	1	1
1	1	0	0	0	1	0
1	1	0	1	0	1	1
1	1	1	0	0	1	1
1	1	1	1	1	0	0

(b) $z_1 = abcd$

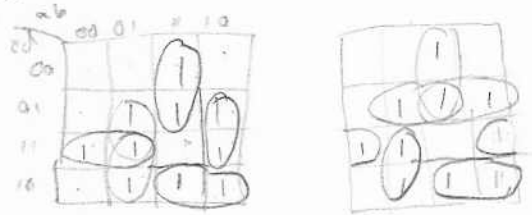

need 6 terms:
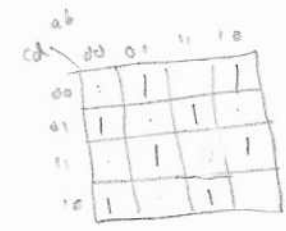
$$z_2 = abc'd + ab'd + a'b'd + a'bc + a'cd + acd'$$



$$z_3 = a'b'c'd + a'b'cd' + a'bc'd' + a'bcd + ab'c'd' + ab'cd + abc'd + abcd'$$

